

## Lab 1. Introduction to modelling

Name: Li Xin

ITMO ID:22320404

Specialization: Automation

### Objective

Familiarize yourself with the Simulink software environment and basic methods for modeling linear electrical circuits.

### Theoretical information

A mathematical model of a linear electric circuit as a linear stationary system can be represented in the form of a scalar differential equation of the  $n$ th order (input-output model) or in the form of a system of  $n$  differential equations of the 1st order (input-state-output model).

The input-output model has the form

$$y^{(n)} + a_{n-1}y^{(n-1)} + \dots + a_1\dot{y} + a_0y = b_mu^{(m)} + b_{m-1}u^{(m-1)} + \dots + b_1\dot{u} + b_0u, \quad (1)$$


where  $y$  is the output variable,  $u$  is the input signal,  $n$  is the order of the system,  $m$  is the order of the derivative of the output variable, which explicitly depends on  $u$  ( $m \leq n$ ),  $a_j, b_j$  are constant coefficients.

Provided that  $m \leq n$ , the input-state-output model can be represented as

$$\begin{cases} \dot{x}_1 = \alpha_{11}x_1 + \alpha_{12}x_2 + \dots + \alpha_{1n}x_n + \beta_1u, \\ \dot{x}_2 = \alpha_{21}x_1 + \alpha_{22}x_2 + \dots + \alpha_{2n}x_n + \beta_2u, \\ \dots \\ \dot{x}_n = \alpha_{n1}x_1 + \alpha_{n2}x_2 + \dots + \alpha_{nn}x_n + \beta_nu, \\ y = c_1x_1 + c_2x_2 + \dots + c_nx_n, \end{cases} \quad (2)$$


where  $x_j$  are the coordinates of the state vector,  $\alpha_{ij}$  and  $\beta_j$  are constant coefficients. System (2) can be represented in a compact vector-matrix form

**Schemes**

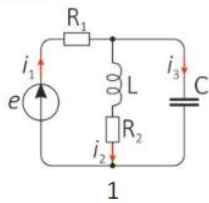


Option	Scheme	Circuit parameters				Source voltage waveform $\omega=50 \cdot 2 \cdot \pi$
		$R_1$ , [Ohm]	$R_2$ , [Ohm]	L, [mH]	C, [uF]	
6	1	12	15	20	10	$e(t) = 24, e(t) = E_m \sin(\omega t)$
6	$W_1(s) = \frac{I_2(s)}{E(s)},$ $W_2(s) = \frac{U_C(s)}{E(s)}$	$x = [I_2 \ U_C]^T$			$x = [1 \ 1]^T$	

**1. Build a simulation circuit.**

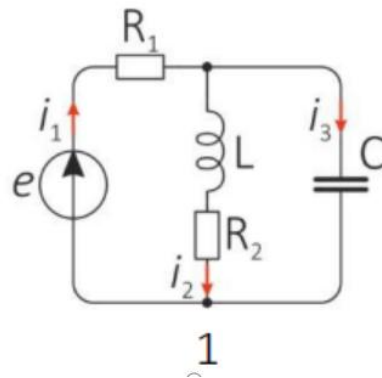

**Figure 1.** Equivalent circuit.

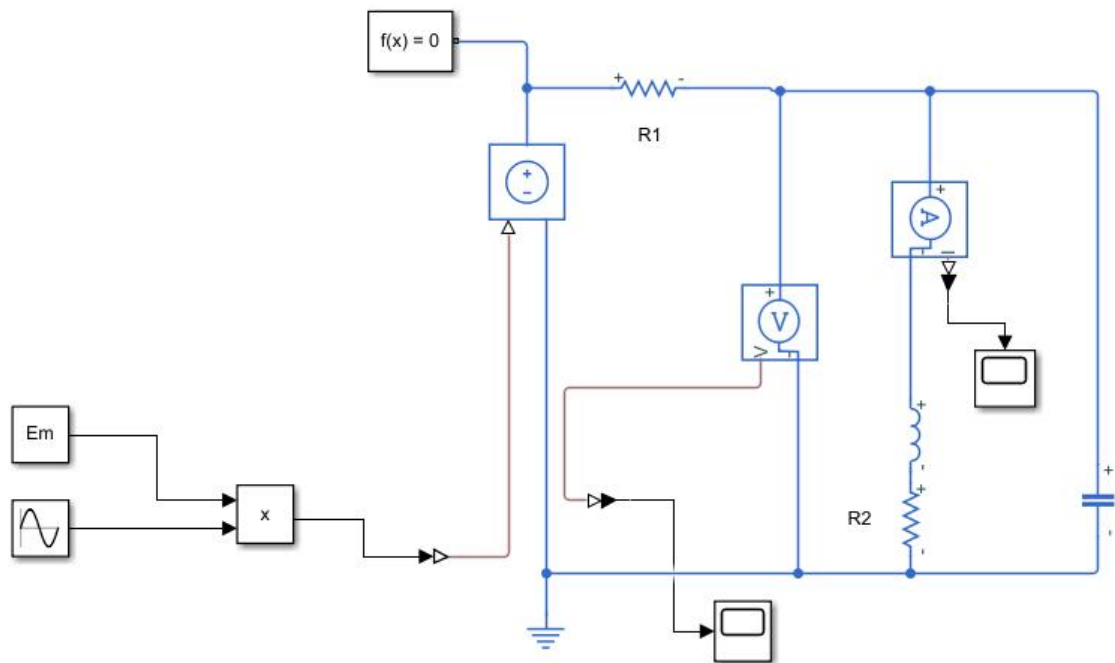

**Figure 2.** Simulation circuit.

## 2. Component equations.

$$\frac{dU_C}{dt} = \frac{I_C}{C}$$

$$U_R = R \cdot I_R$$

$$U_L = L \frac{dI_L}{dt}$$

## 3. Topological equations.

$$e(t) - u_{R1} - u_L - u_{R2} = 0$$

$$u_L + u_{R2} - u_C = 0$$

$$i_1 = i_2 + i_3$$

## 4. State-space model.

$$\frac{dx_1}{dt} = \frac{di_2}{dt}, \quad \frac{dx_2}{dt} = \frac{du_C}{dt}$$

$$e(t) = u_{R1} + u_C = i_1 R_1 + u_C = \left( C \frac{du_C}{dt} + i_2 \right) R_1 + u_C$$

$$e(t) = CR_1 \frac{du_C}{dt} + i_2 R_1 + u_C$$

$$\frac{du_C}{dt} = \frac{e(t) + i_2 R_1 - u_C}{CR_1} = -\frac{1}{C} i_2 - \frac{1}{CR_1} u_C + \frac{e(t)}{CR_1}$$

**Solution:**  $a_{12} = -\frac{1}{C}, \quad a_{22} = -\frac{1}{CR_1}, \quad b_{21} = \frac{1}{CR_1}$

$$\frac{di_2}{dt} = \frac{u_L}{L} = \frac{u_C - i_2 R_2}{L} = -\frac{R_2}{L} i_2 + \frac{1}{L} u_C$$

**Solution:**  $a_{11} = -\frac{R_2}{L}, \quad a_{12} = \frac{1}{L}, \quad b_{11} = 0$

5. Simulink simulation of the circuit and the state-space model using the predetermined input and zero initial conditions.



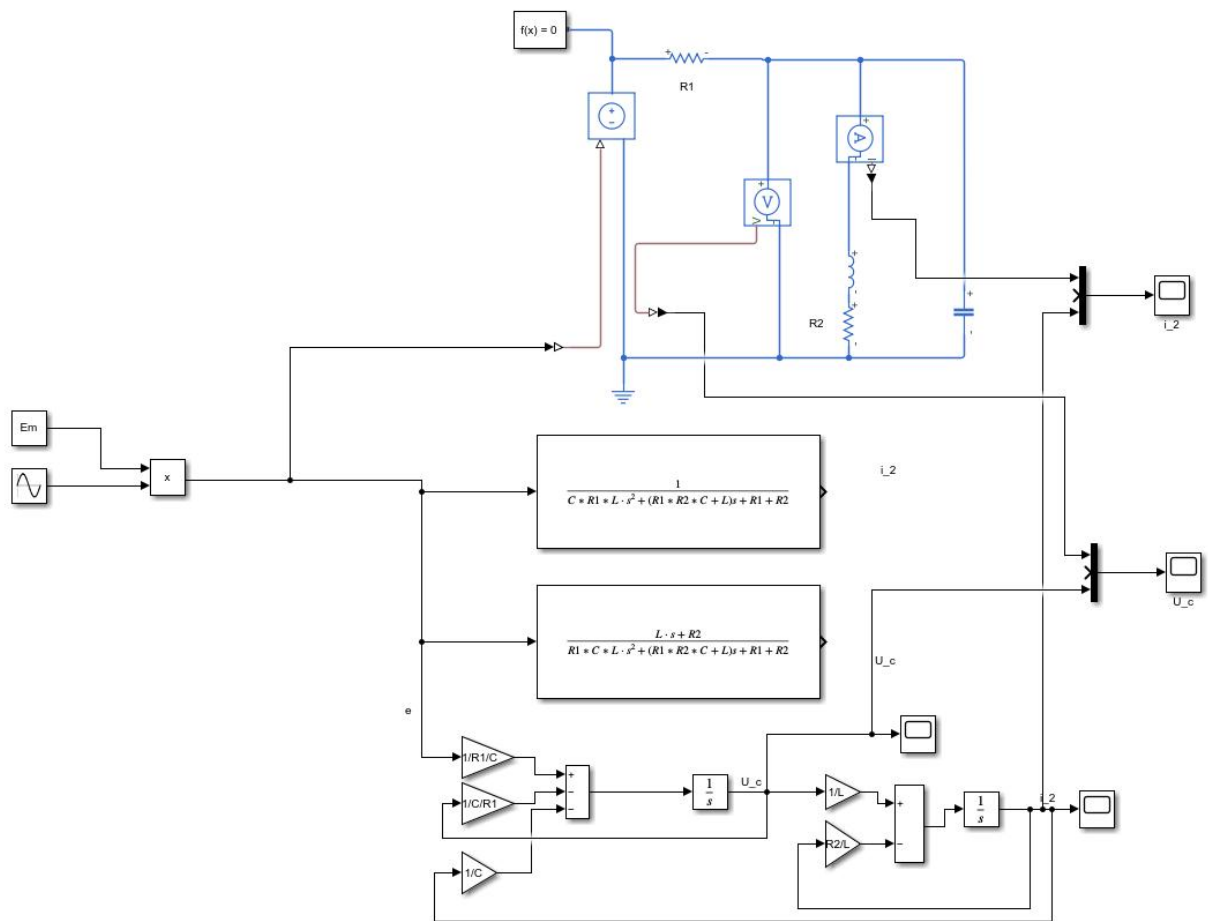



Figure 3 Modelling with sinusoidal input voltage

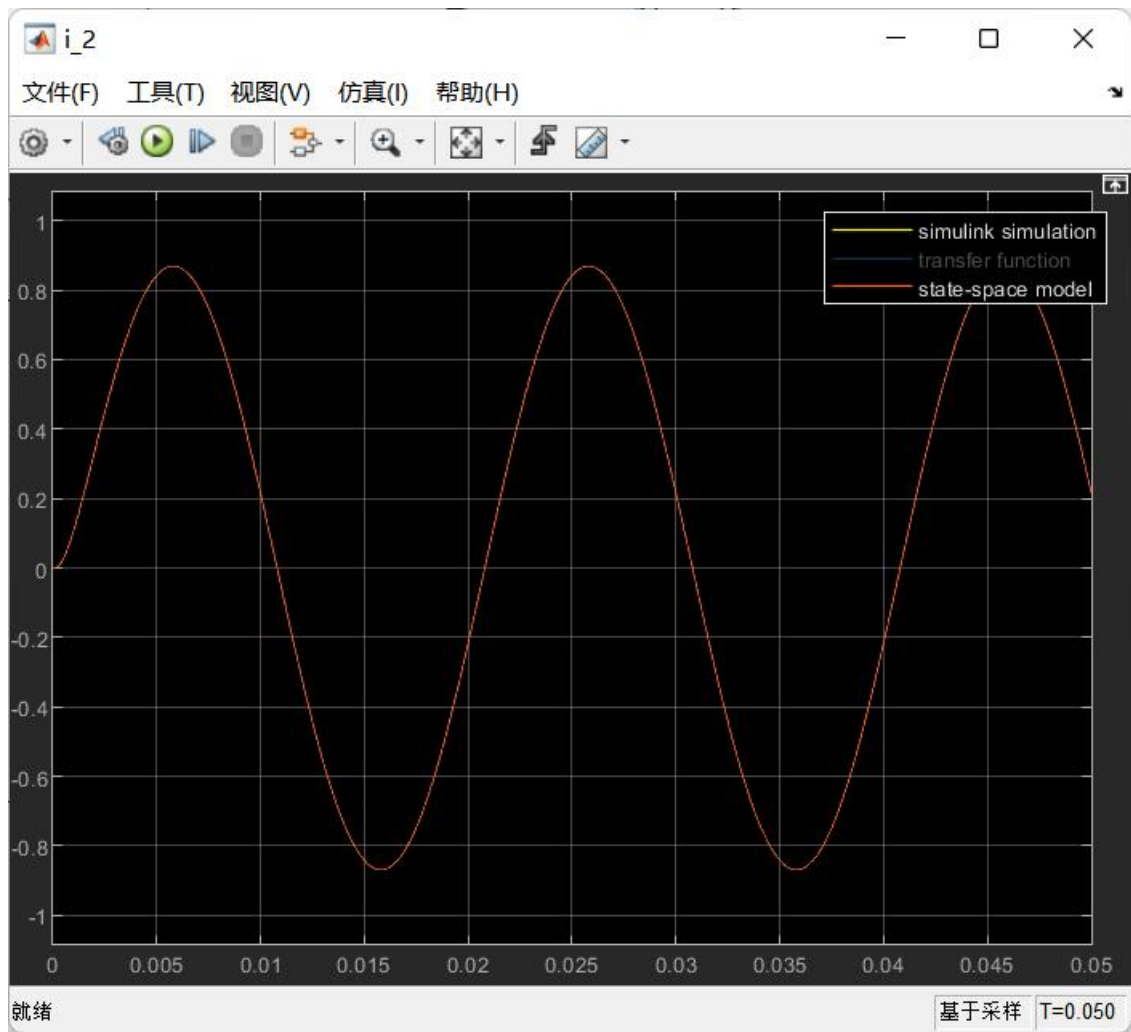


**Figure 4** i\_2 of Simulink simulation of the circuit and the state-space model

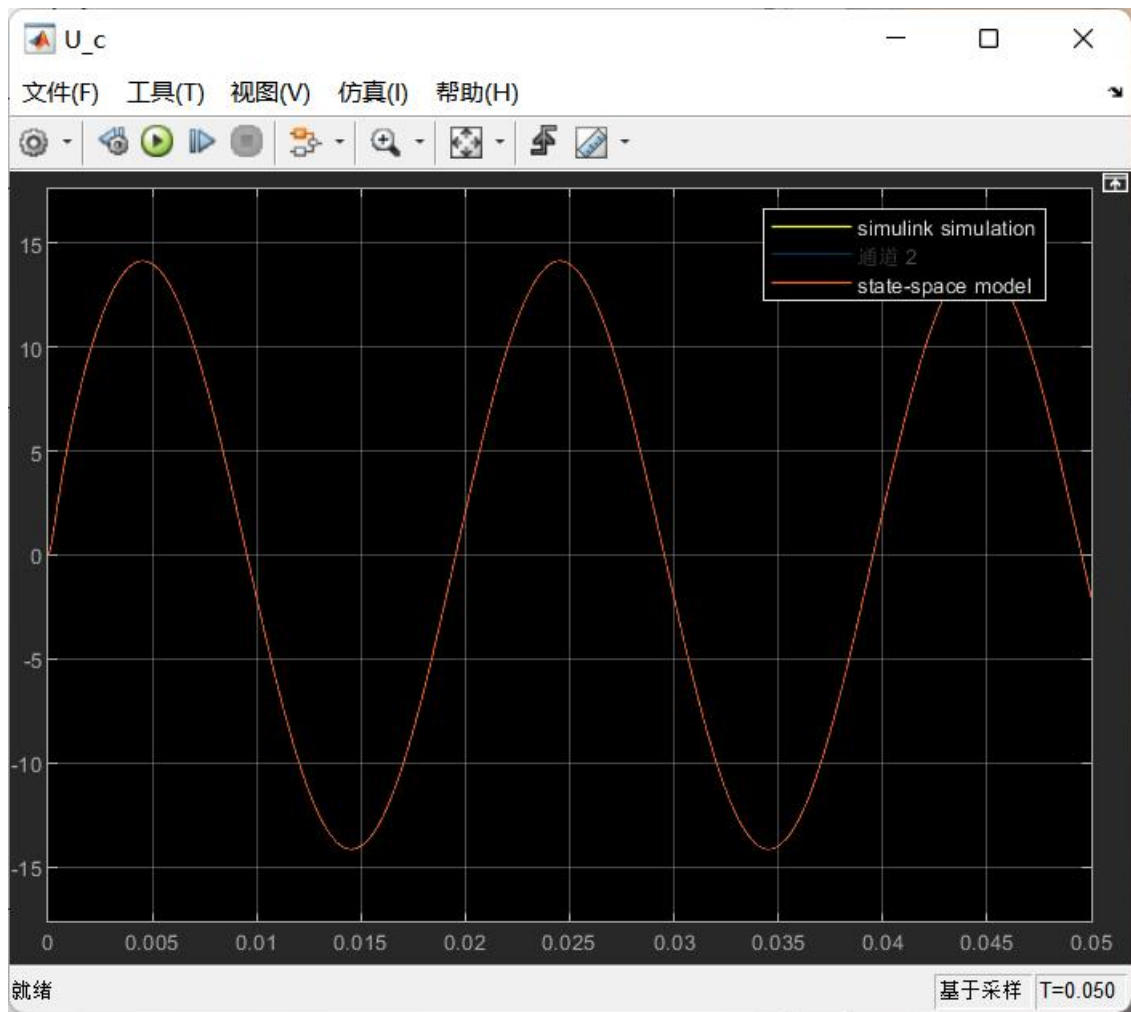

**Figure 5**  $U_c$  of Simulink simulation of the circuit and the state-space model

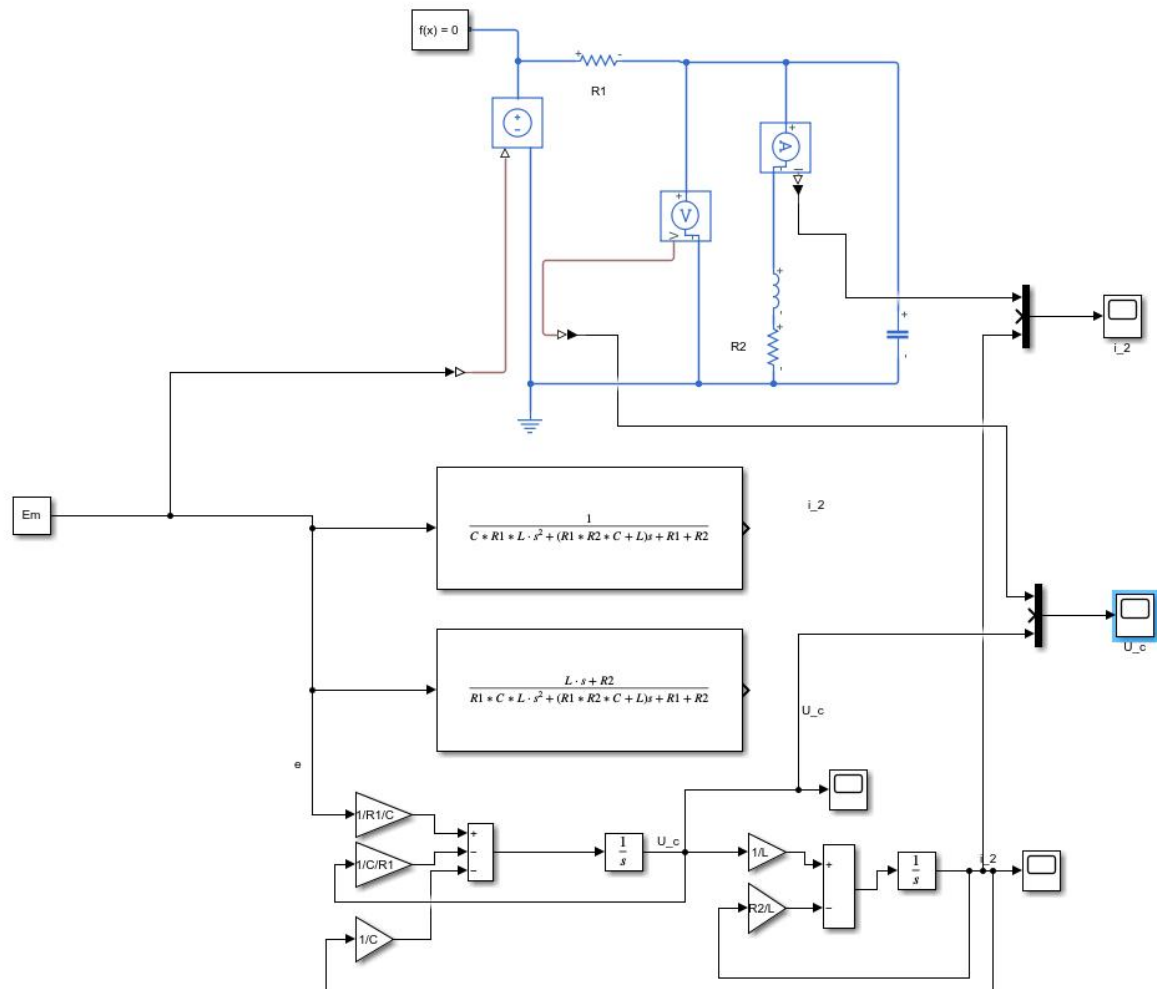


**Figure 6** Modelling with constant voltage

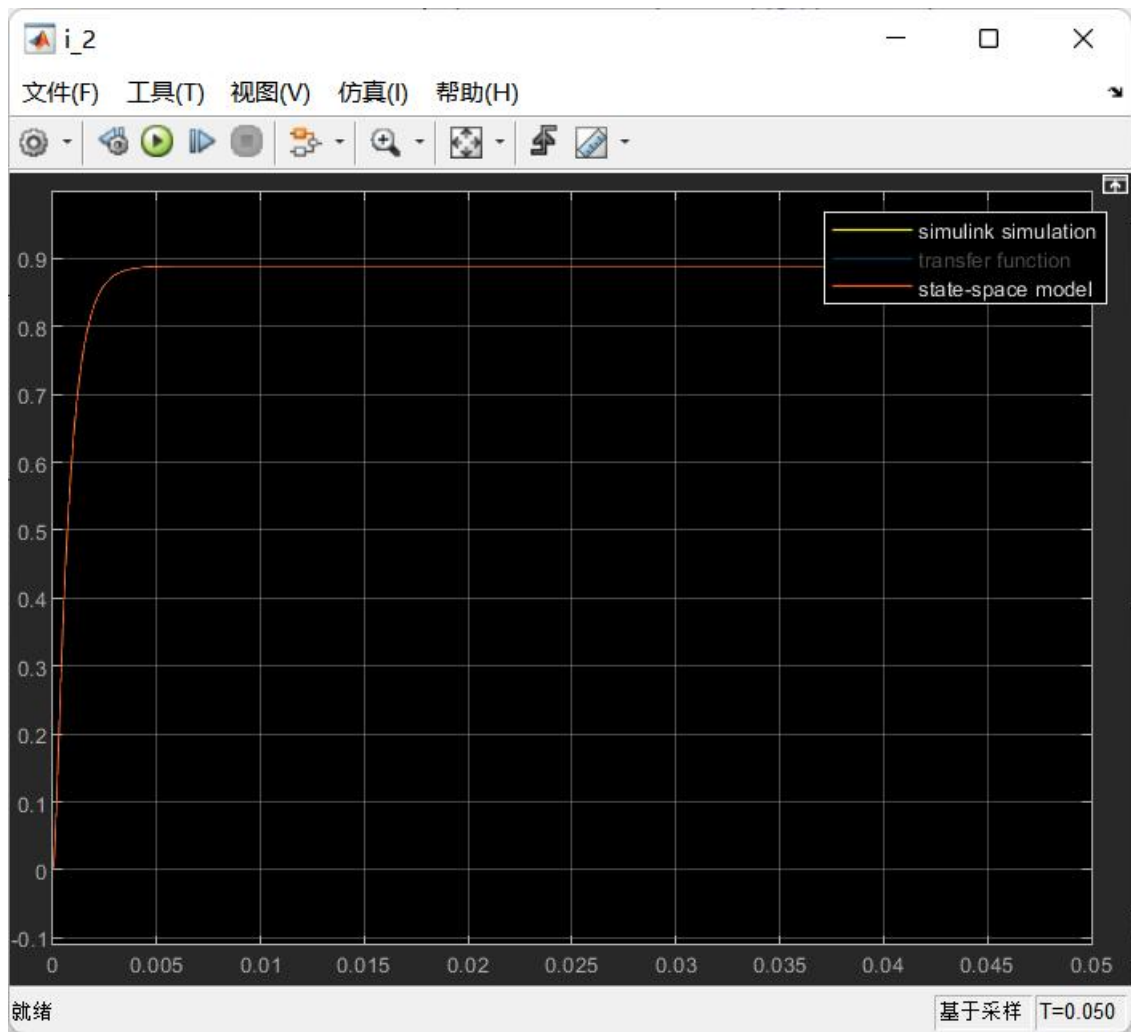

**Figure 7**  $i_2$  of Simulink simulation of the circuit and the state-space model



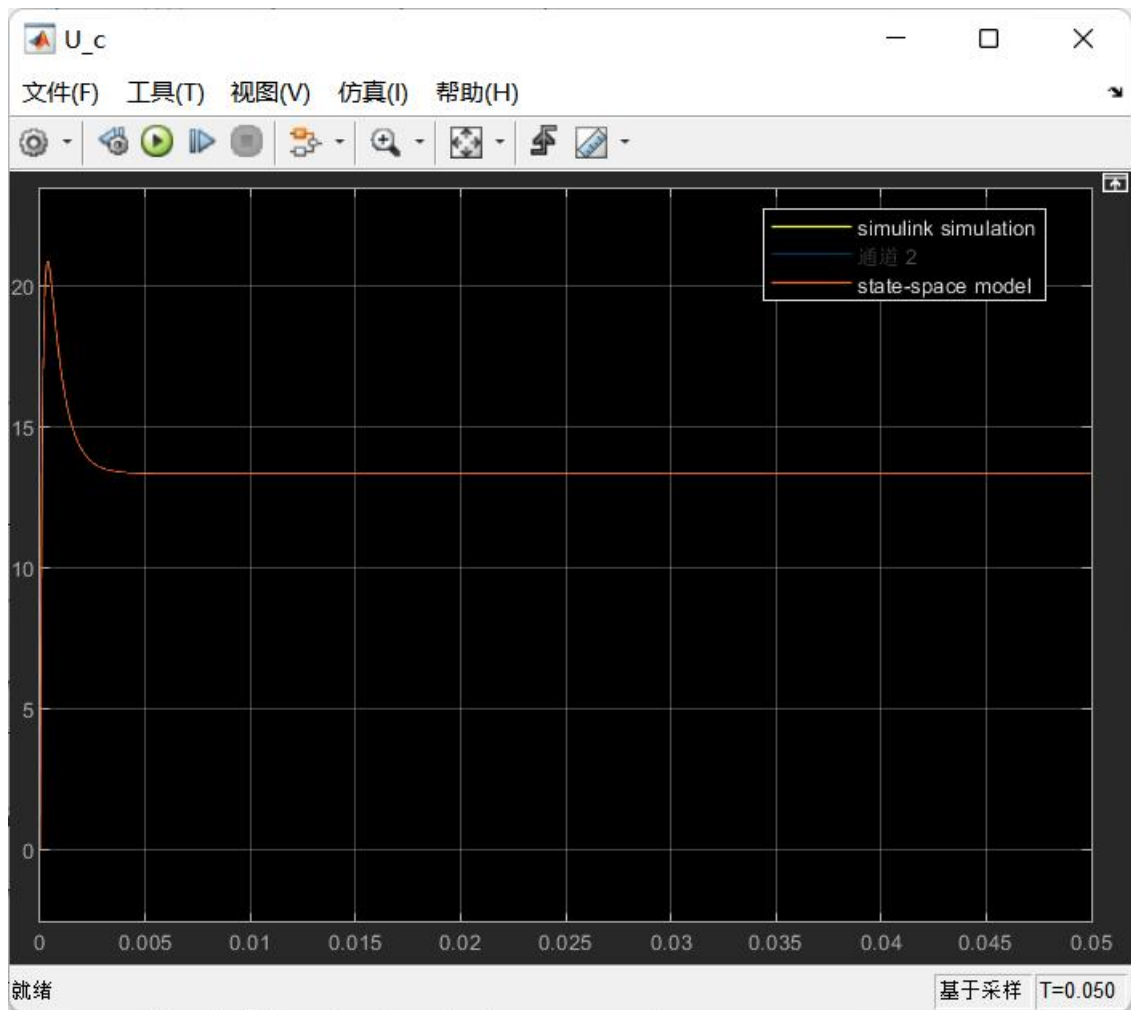

**Figure 8**  $U_c$  of Simulink simulation of the circuit and the state-space model


## 6. "Input-output" model.

$$s i_2 = \frac{U_C - i_2 R_2}{L}$$


$$s U_C = -\frac{i_2}{C} - \frac{U_C}{C R_1} + \frac{1}{C R_1} e$$

$$U_C(s) = \frac{L S + R_2}{C R_1 L S^2 + (C R_1 R_2 + L) S + R_1 + R_2} e(s)$$

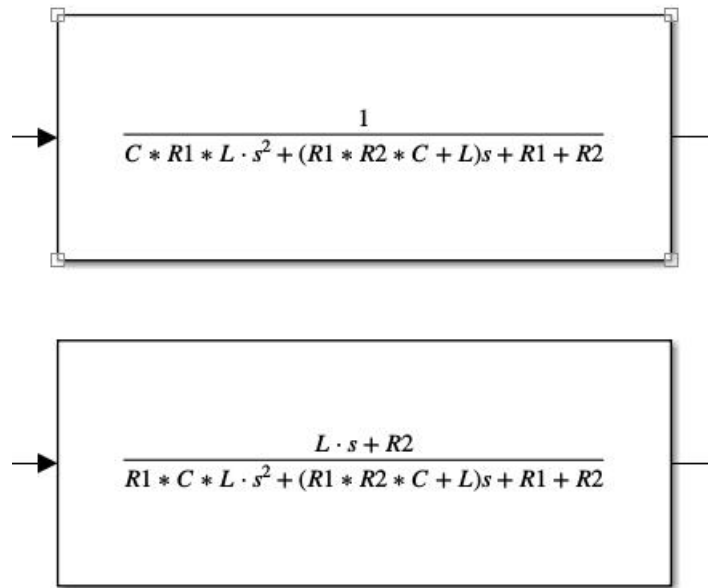
$$i_2(s) = \frac{1}{C R_1 L S^2 + (C R_1 R_2 + L) S + R_1 + R_2} e(s)$$




## 7. Simulink simulation of the circuit and the resulting transfer functions using the predetermined input

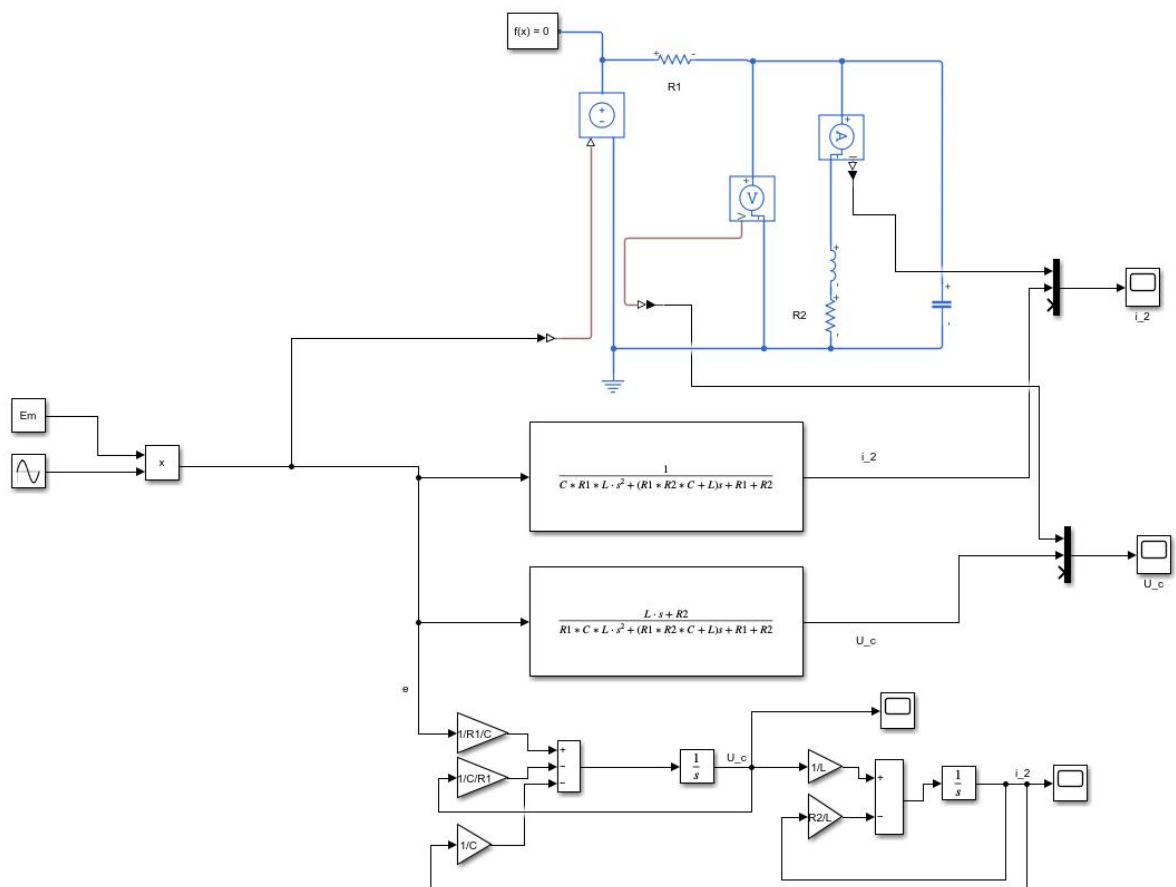


**Figure 9** Modelling with sinusoidal input voltage

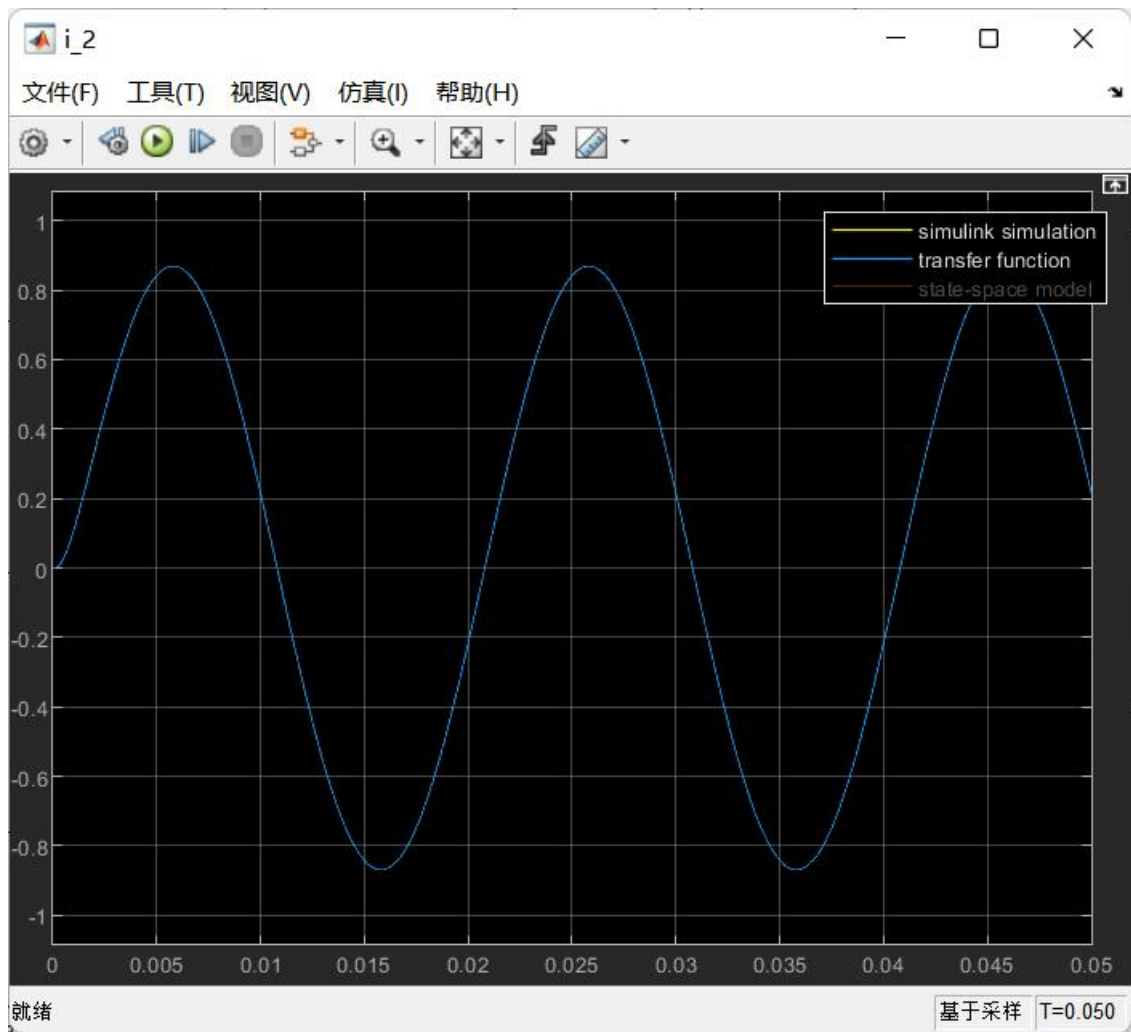


**Figure 10** i\_2 of Simulink simulation of the circuit and transfer functions

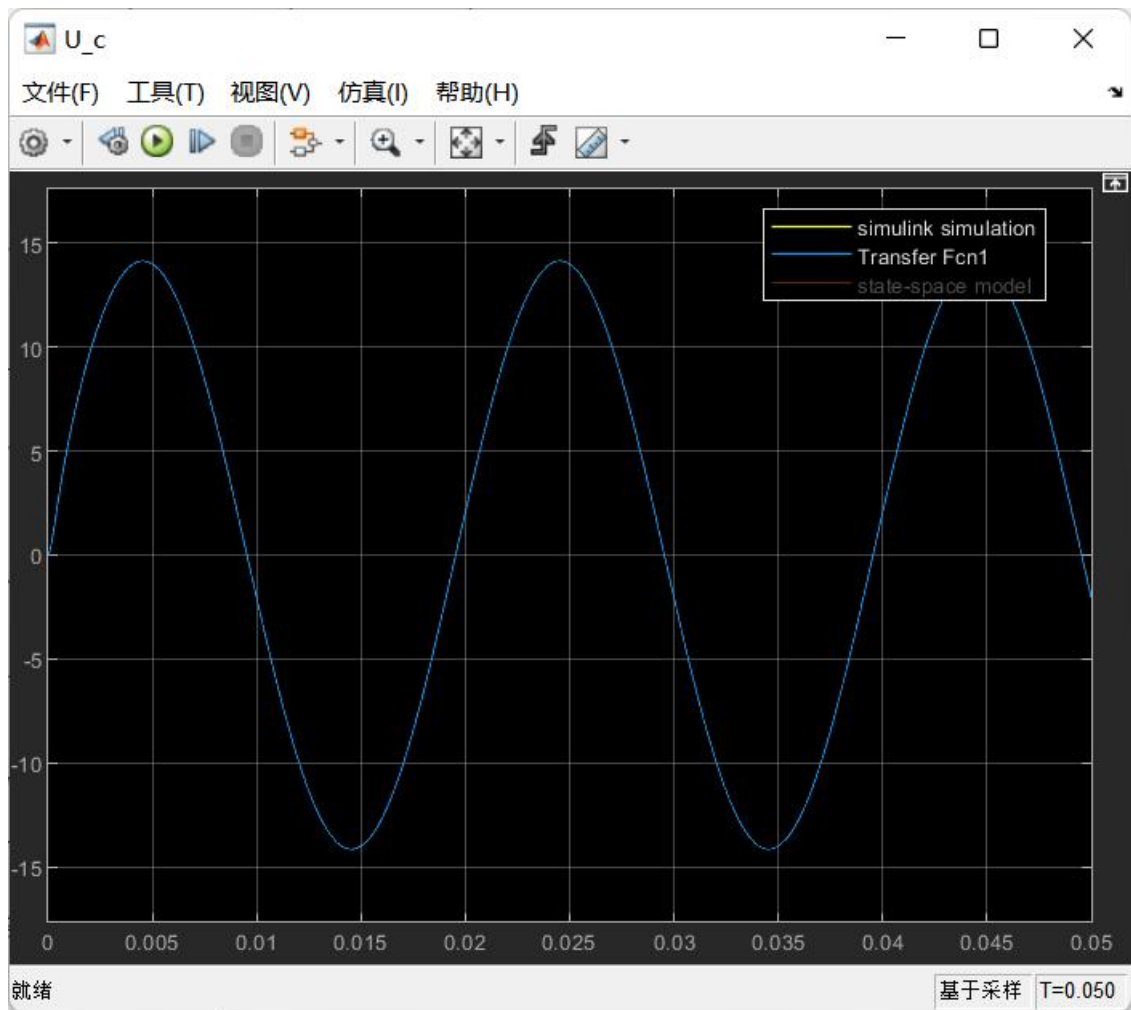


**Figure 11**  $U_c$  of Simulink simulation of the circuit and transfer functions

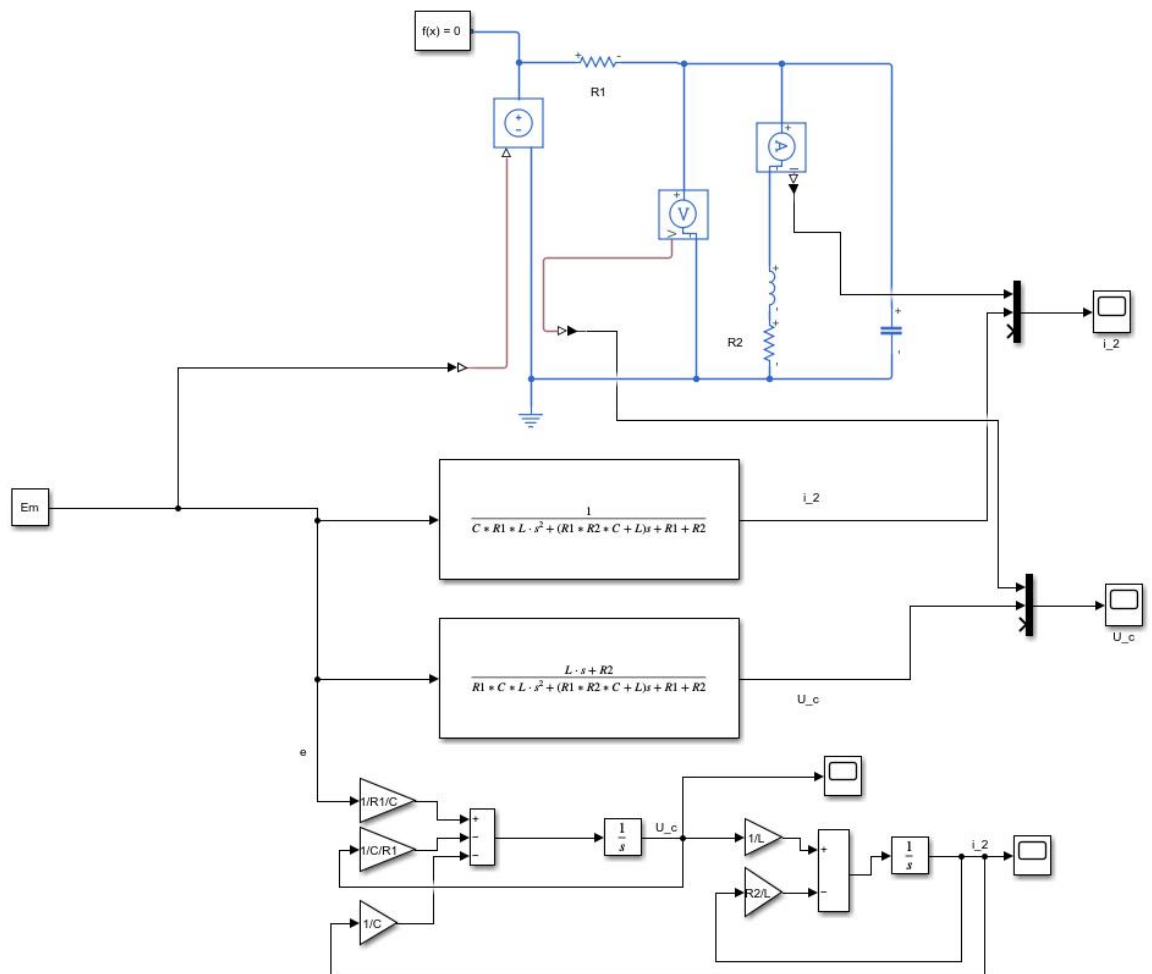

**Figure 12** Modelling with constant voltage

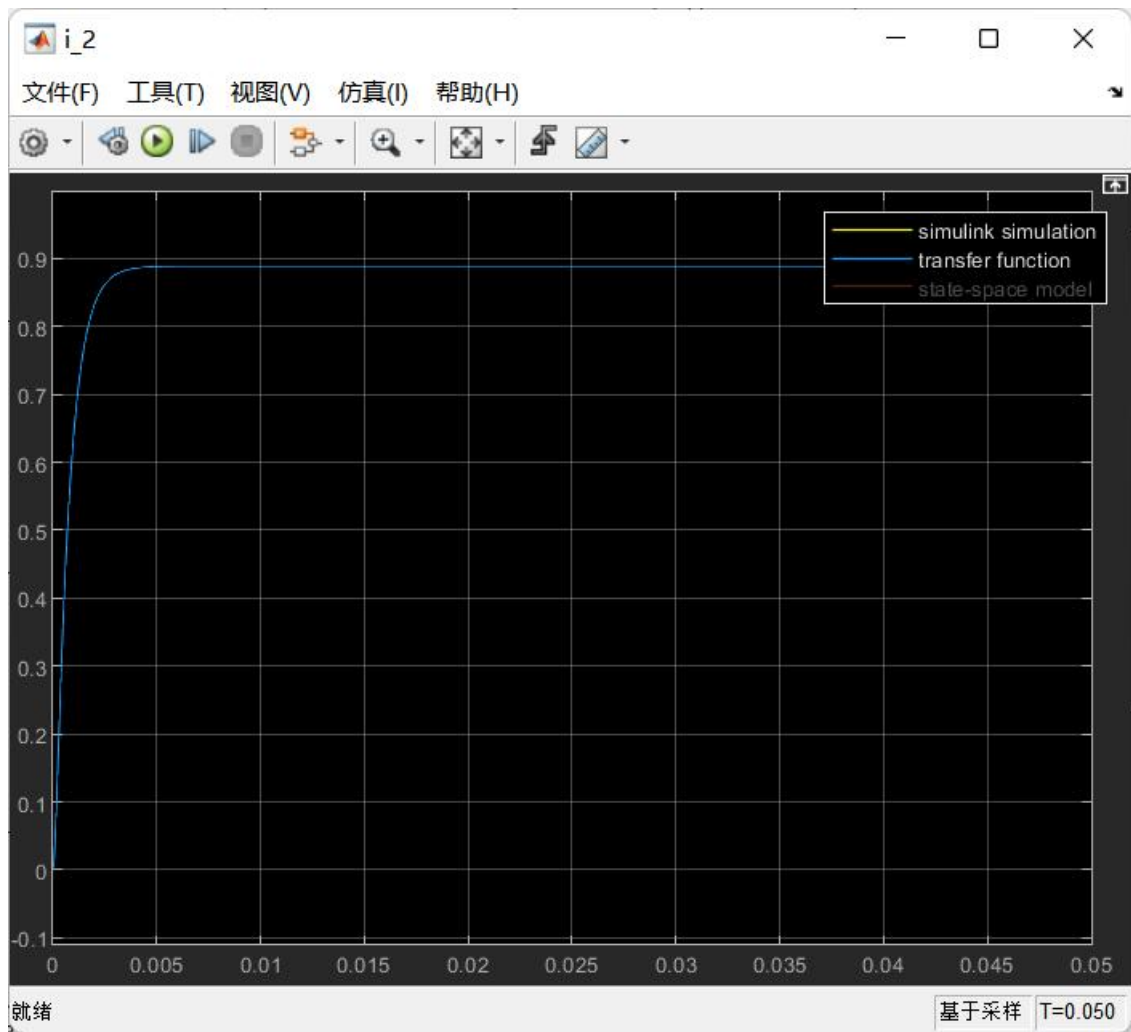


**Figure 13** i\_2 of Simulink simulation of the circuit and transfer functions

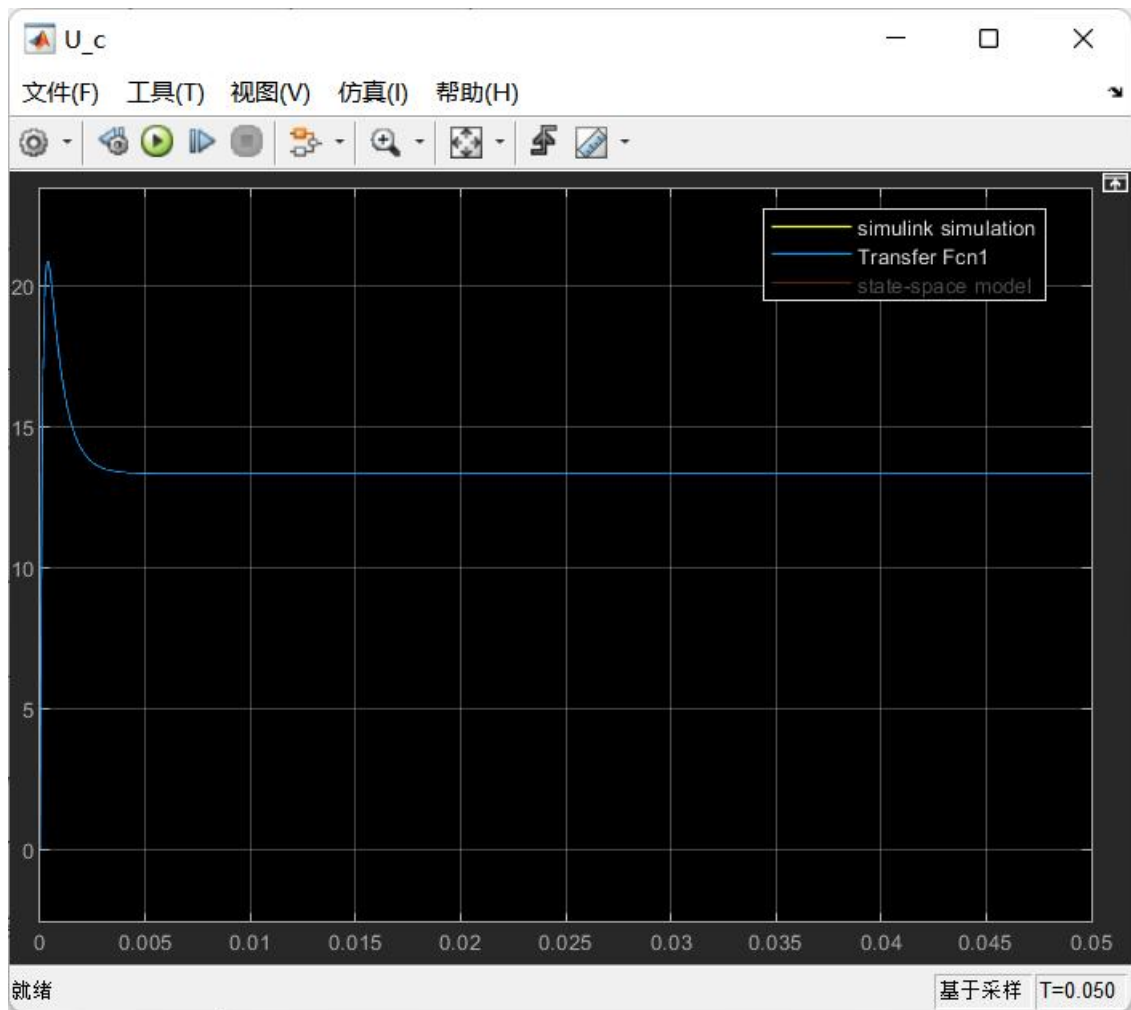


**Figure 14**  $U_c$  of Simulink simulation of the circuit and transfer functions

**8. Simulation of the circuit and the state-space model with zero input and non-zero initial conditions.**

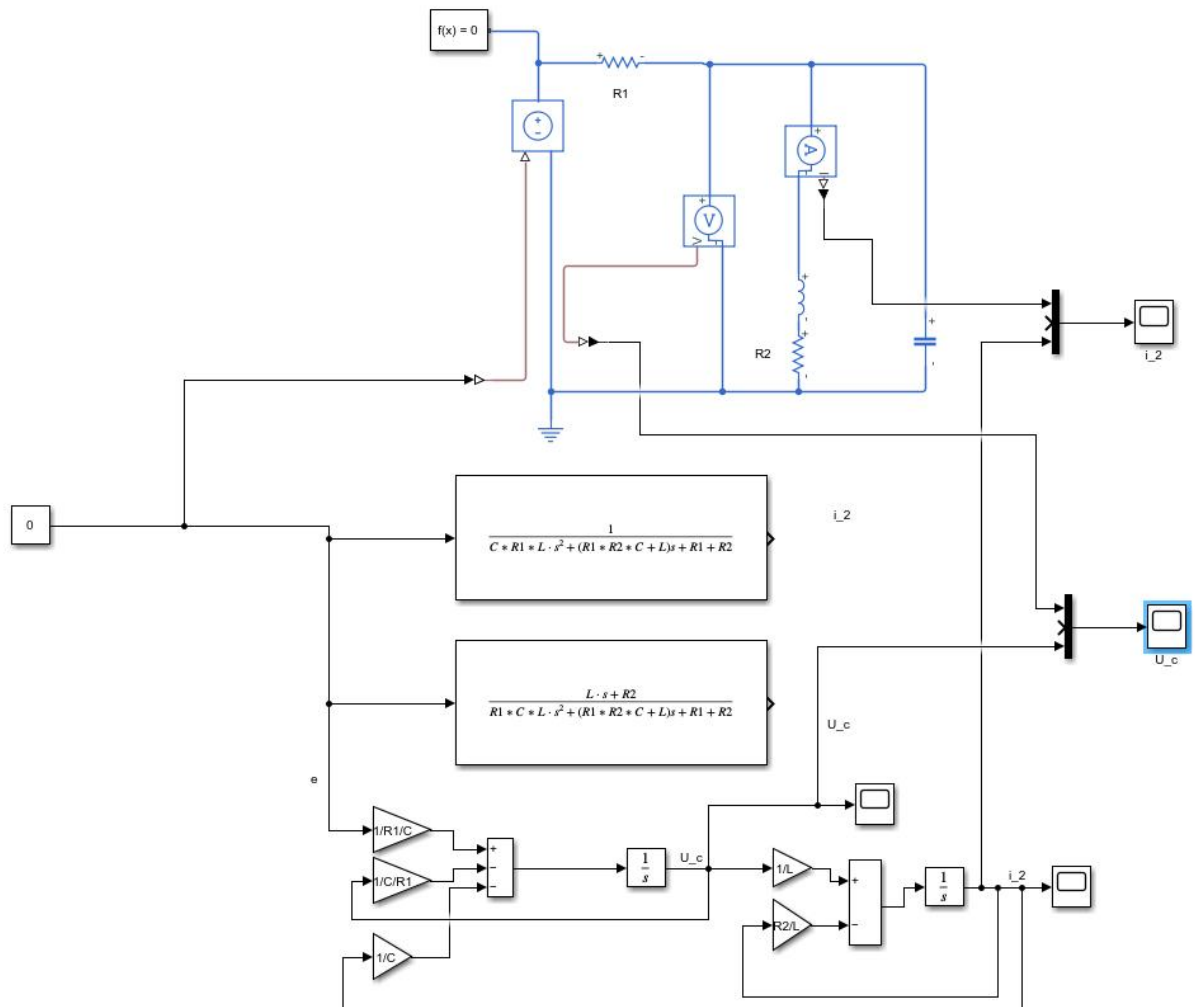


**Figure 15** Modelling with zero voltage and nonzero initial conditions



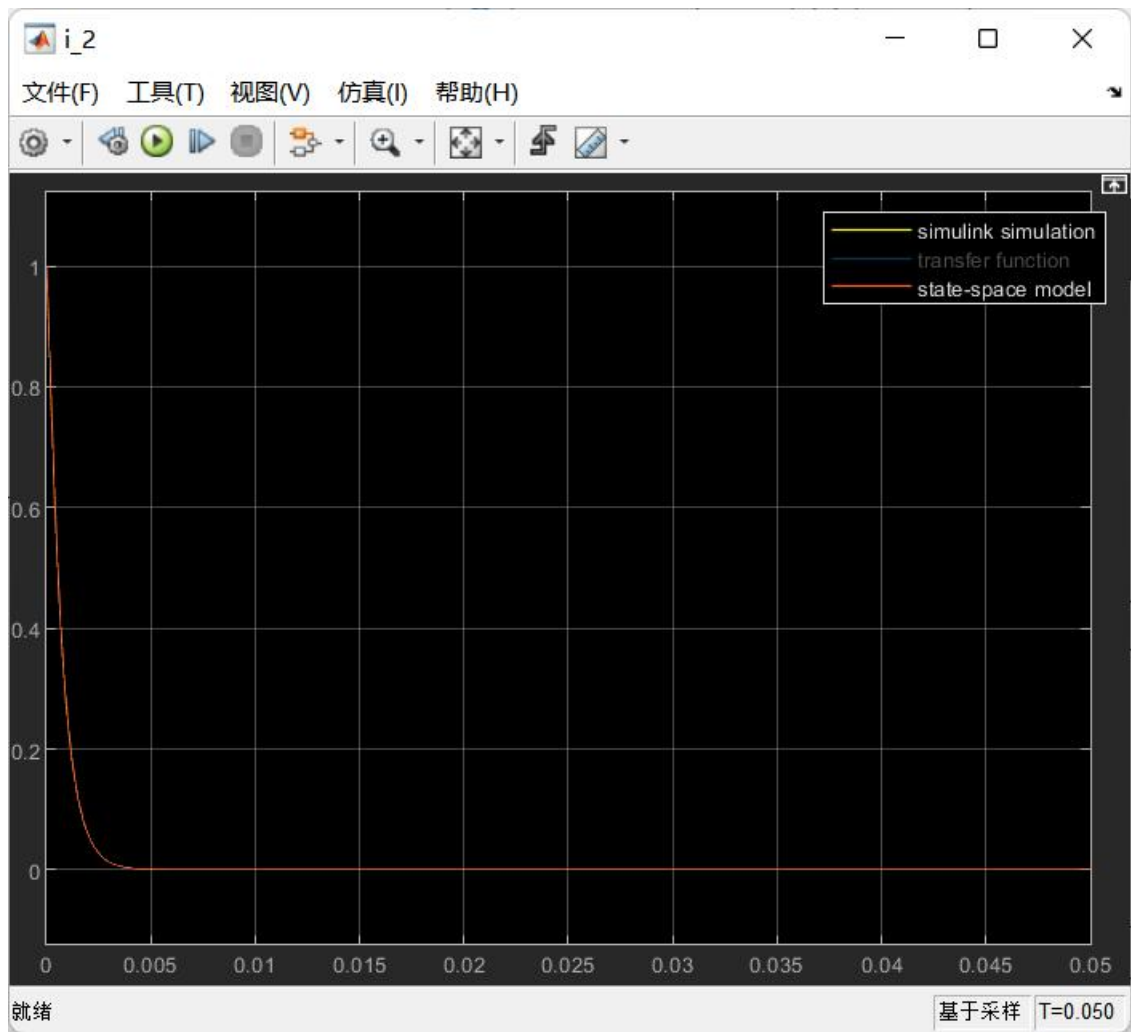

**Figure 16** i\_2 of Simulink simulation of the circuit and the state-space model

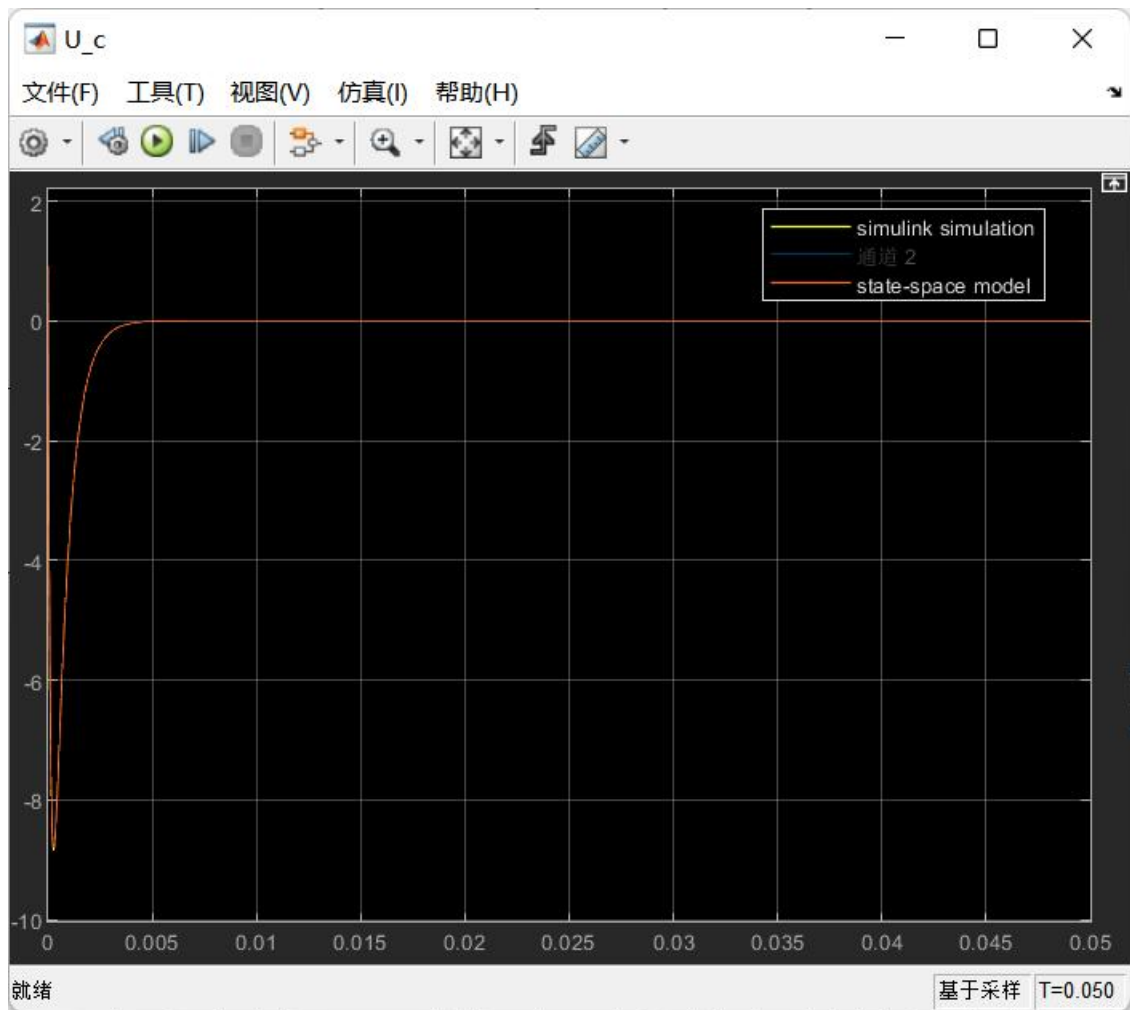

**Figure 17**  $U_c$  of Simulink simulation of the circuit and the state-space model

## Conclusions:

In this lab, I successfully implemented and simulated a linear electrical circuit using three different modeling approaches in Simulink: Simscape circuit, state-space representation, and transfer function.

Through the experiments, I observed that all three models produced similar transient and steady-state responses, confirming their theoretical equivalence in circuit analysis.

And I applied different types of input signals to the circuit, including sinusoidal voltage, constant voltage, and zero input with nonzero initial conditions. For sinusoidal voltage, The circuit responded with a steady-state sinusoidal output, maintaining the same frequency as the input but with an amplitude change and a phase shift. For constant voltage, The circuit exhibited transient behavior before reaching a steady-state condition. For zero input with nonzero initial conditions, I observed the system's natural response, which depends entirely on the circuit's initial energy stored in capacitors and inductors.

